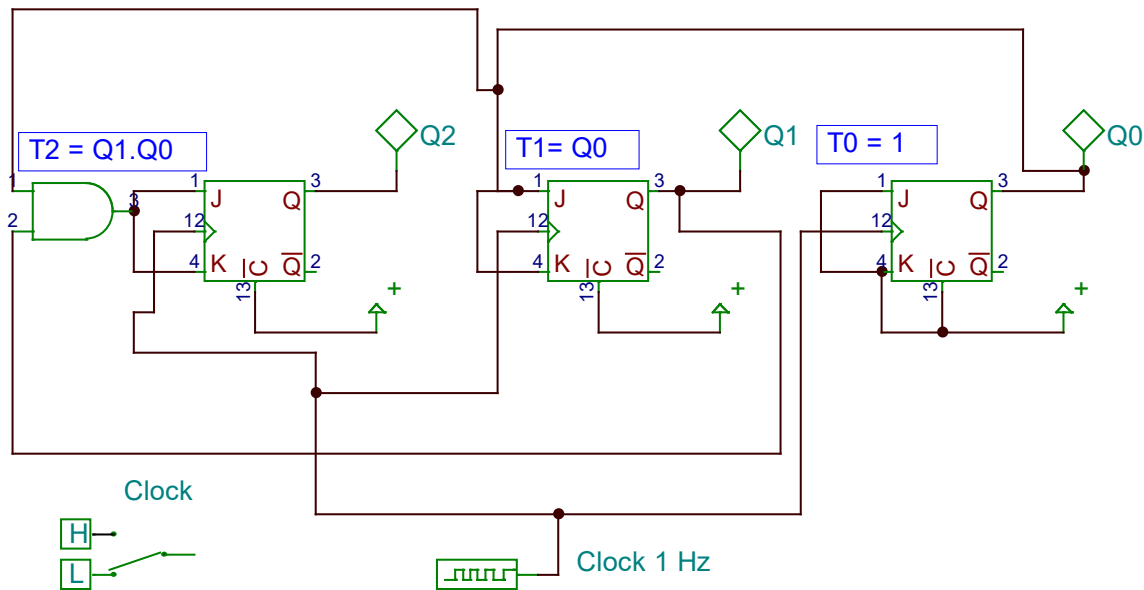


10-22-25 Lecture on: Flip Flop and Binary Counters.

Applications for FF: Static memory, Binary counters, Sequence detector

Electronic latch



Count	Q2	Q1	Q0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

$$T = f(Q0, Q1, Q2)$$

Q2	0	1
Q1Q0		
00	1	1
01	1	1
11	1	1
10	1	1

T	Qt+1
0	NC
1	Toggle

$$T0 = 1$$

Count	Q2	Q1	Q0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

$T = f(Q0, Q1, Q2)$

Q2 Q1Q0	0	1
00	0	0
01	1	1
11	1	1
10	0	0

$T1 = Q0$

T	Qt+1
0	NC
1	Toggle

Count	Q2	Q1	Q0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

$T = f(Q_0, Q_1, Q_2)$

Q2 Q1Q0	0	1
00	0	0
01	0	0
11	1	1
10	0	0

$T_2 = Q_1.Q_0$

$T_{Q_{t+1}}$

0 NC

1 Toggle

Design a binary counter that counts → 0,5,2,3,4,7 and back to 0

Count	Q2	Q1	Q0
0	0	0	0
5	1	0	1
2	0	1	0
3	0	1	1
4	1	0	0
7	1	1	1

$T_0 = 1$

$2^{\#FF} \geq \text{Counting states}$

Q2	0	1
Q1Q0		
00	0	1
01	d	1
11	1	1
10	0	d

$T_1 = Q_0 + Q_2$

Count	Q2	Q1	Q0
0	0	0	0
5	1	0	1
2	0	1	0
3	0	1	1
4	1	0	0
7	1	1	1

Q2	0	1
Q1Q0		
00	1	0
01	d	1
11	1	1
10	0	d

$T_2 = Q_0 + Q_2' \cdot Q_1'$

Schematic for the counter that counts 0,5,2,3,4,7 and back to 0

