

Classwork # 2.

Make sure that I verify receiving your email to prof@dpeled.com

1. Simplify the following K-maps. Draw the final simplified circuit.

Use a Circuit Simulator to draw the circuit.

| AB CD | 00 | 01 | 11 | 10 |
|----------|----|----|----|----|
| 00 | 1 | | | 1 |
| 01 | | 1 | 1 | |
| 11 | 1 | 1 | 1 | 1 |
| 10 | | 1 | 1 | |

| AB CD | 00 | 01 | 11 | 10 |
|----------|----|----|----|----|
| 00 | 1 | 1 | | 1 |
| 01 | 1 | 1 | 1 | 1 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | 1 | 1 | 1 | 1 |

GOOD LUCK!

2. Obtain the Boolean algebra equation from a circuit,

- simplify it and redraw the simplified circuit.

