

# Quiz NO4

One hour.

Simplify the following three K-Amps. Draw the final simplified circuit using Tina and send the image with the simplified expression to prof@dpeled.com  
If you cannot save the circuit on Tina then copy and paste it onto Word or email.

AB CD	00	01	11	10
00	1	1		1
01	1	1	1	1
11	1	1	1	1
10	1	1		1

Make sure that I verify receiving your email.

AB CD	00	01	11	10
00	1			1
01		1	1	
11	1	1	1	1
10		1	1	

AB CD	00	01	11	10
00	1			
01		1		
11			1	
10				1

**GOOD LUCK!**