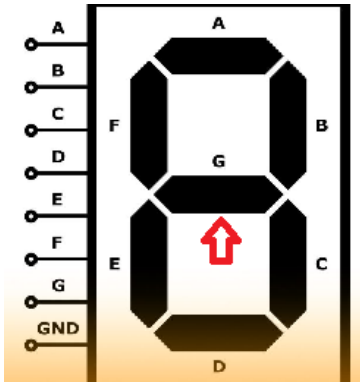



1. Design and implement a 7 segments decoder for the segment g(8).



Count	G(8)
0	0
1	0
2	1
3	1
4	1
5	1
6	1
7	0

W	0	1
XY		
00	0	1
01	0	1
11	1	0
10	1	1

$$G(8) = W'X + WX' + XY' = W(+)X + XY'$$

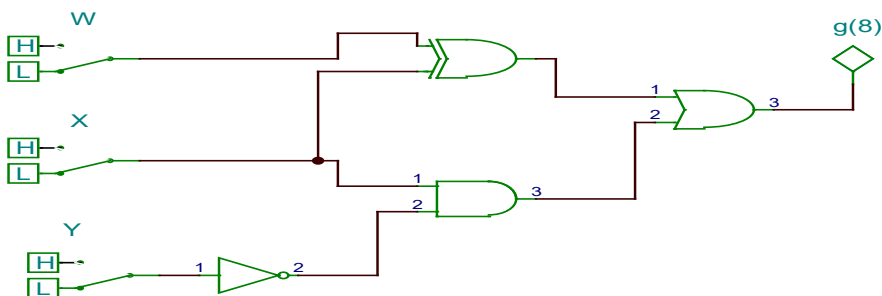

2. Using T-FF Design and implement a synchronous oop counter that counts: $5 \rightarrow 3 \rightarrow 2 \rightarrow 4 \rightarrow 6$.

Count	Q2	Q1	Q0
5	1	0	1
3	0	1	1
2	0	1	0
4	1	0	0
6	1	1	0

Q2 Q1Q0	0	1
00	d	0
01	d	0
11	1	d
10	0	1

$$T_0 = Q_1Q_2 + Q_1Q_0 = Q_1(Q_2+Q_0)$$


Count	Q2	Q1	Q0
5	1	0	1
3	0	1	1
2	0	1	0
4	1	0	0
6	1	1	0

Q2	Q1	Q0
00	d	1
01	d	1
11	0	d
10	1	1

$$T1 = Q2 + Q0'$$

Q2	Q1	Q0
00	d	0
01	d	1
11	0	d
10	1	0

$$T2 = Q2Q0 + Q2'Q0' = (Q2(+)+Q0)'$$

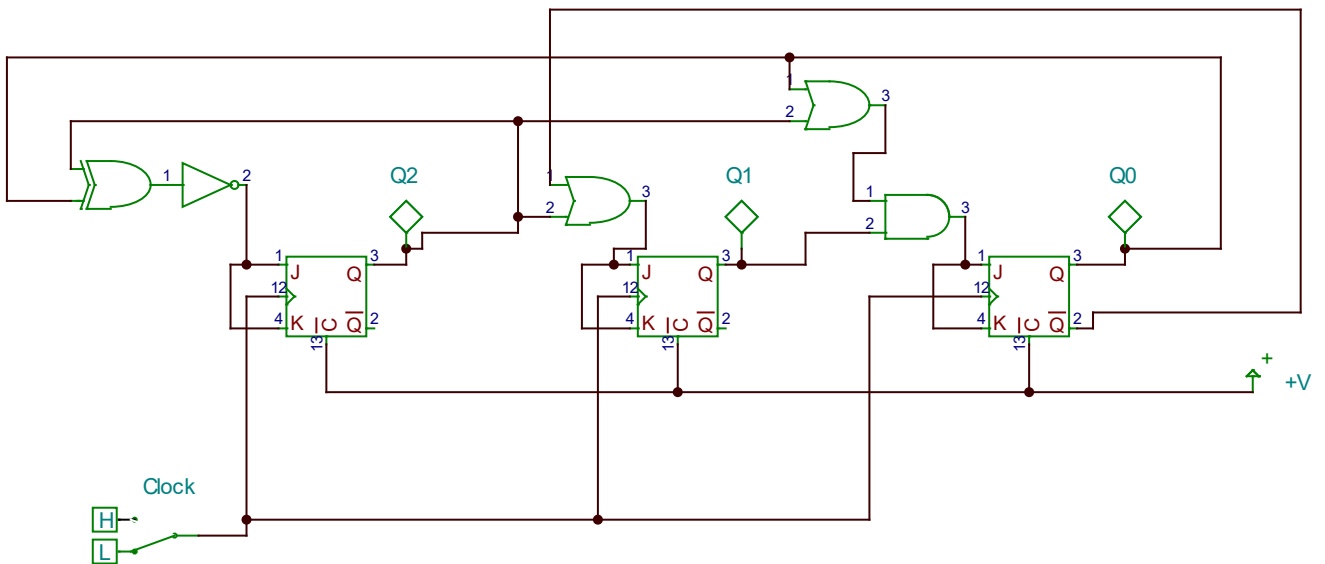

3 Simplify $Y = A(+)B + (D(+)C)' + C'D + ABC$
 $= A'B + AB' + C'D' + CD + C'D + ABC$

AB CD	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	0	1	1	1

$Y' = A'B'CD' \rightarrow Y'' = (A'B'CD')' = A+B+C'+D$